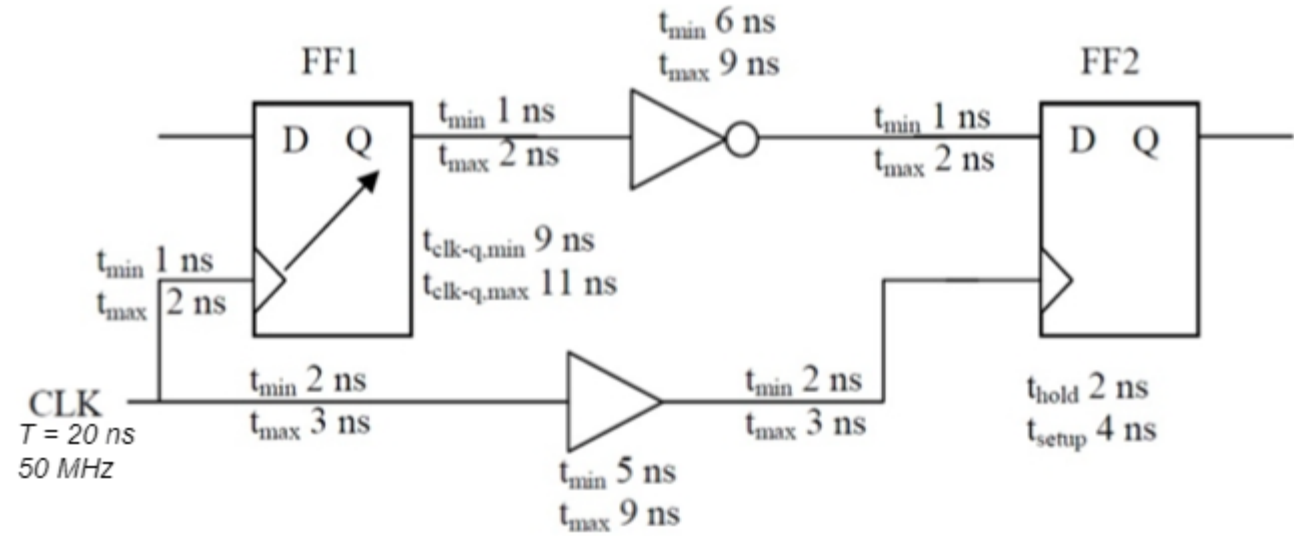


Example: Setup


Calculate Maximum Frequency



Setup slack: $\text{min delay along clock path} - \text{max delay along data path} = 25 - 26 = -1\text{ ns}$


- Setup Slack = -1 ns
- Make the period 1 ns longer, $20+1 = \text{new period} = 21\text{ ns}$
- $T_{\min} = DAT_{\max} + t_{\text{su}} - t_{\text{clk,min}} = 26+4-9=21\text{ ns}$
= Data Arrival Time + setup time of destination reg – clock delay to destination reg
- $f_{\max} = 1/T_{\min} = 1/21 = 47.6\text{ MHz}$

Example: Hold

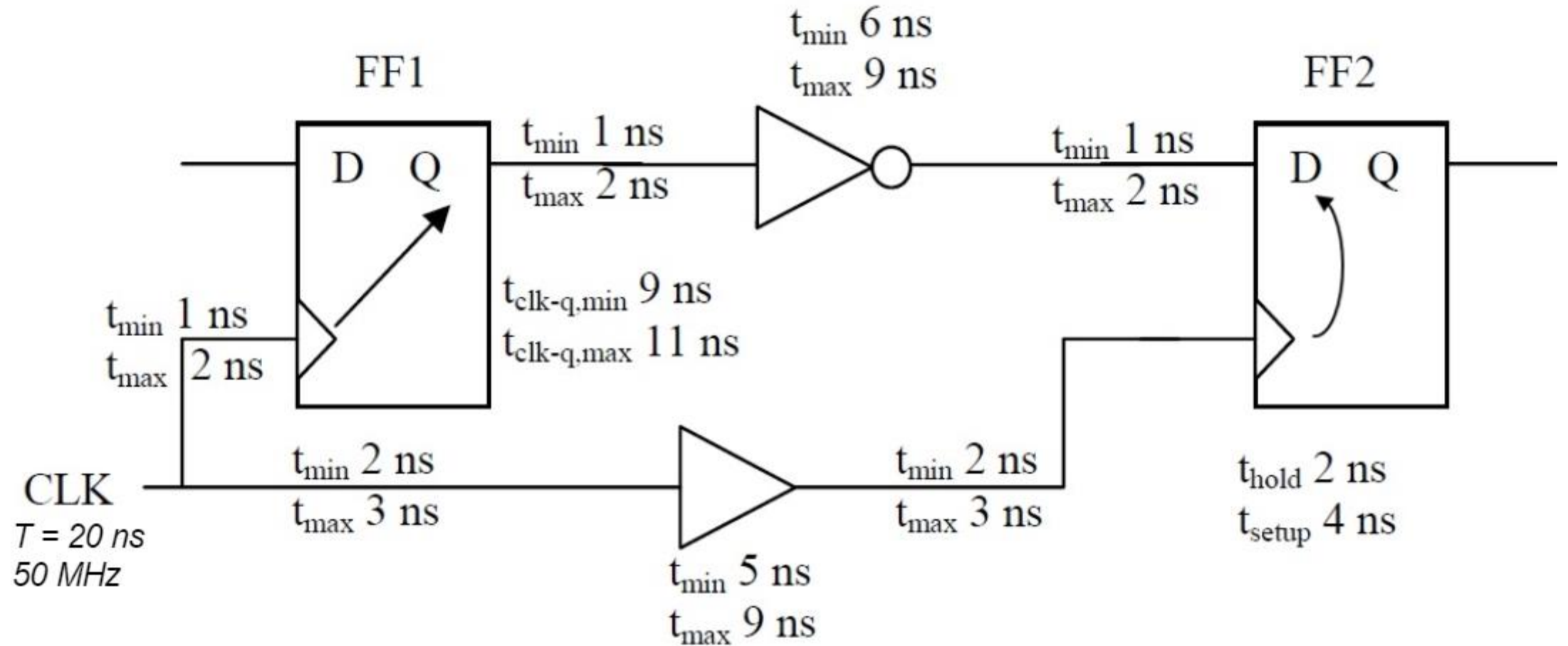


Hold slack: $\text{min delay along data path} - \text{max delay along clock path} =$
(min data arrival time) (max data required time)

Example: Hold

 

Hold slack: min delay along data path – max delay along clock path = (1+9+1+6+1) –
 (min data arrival time) (max data required time)


Example: Hold

 

Hold slack: $\text{min delay along data path (min data arrival time)} - \text{max delay along clock path (max data required time)} = (1+9+1+6+1) - (3+9+3+2) = 18-17 = 1\text{ ns}$

Problem


Exercise 1(a)

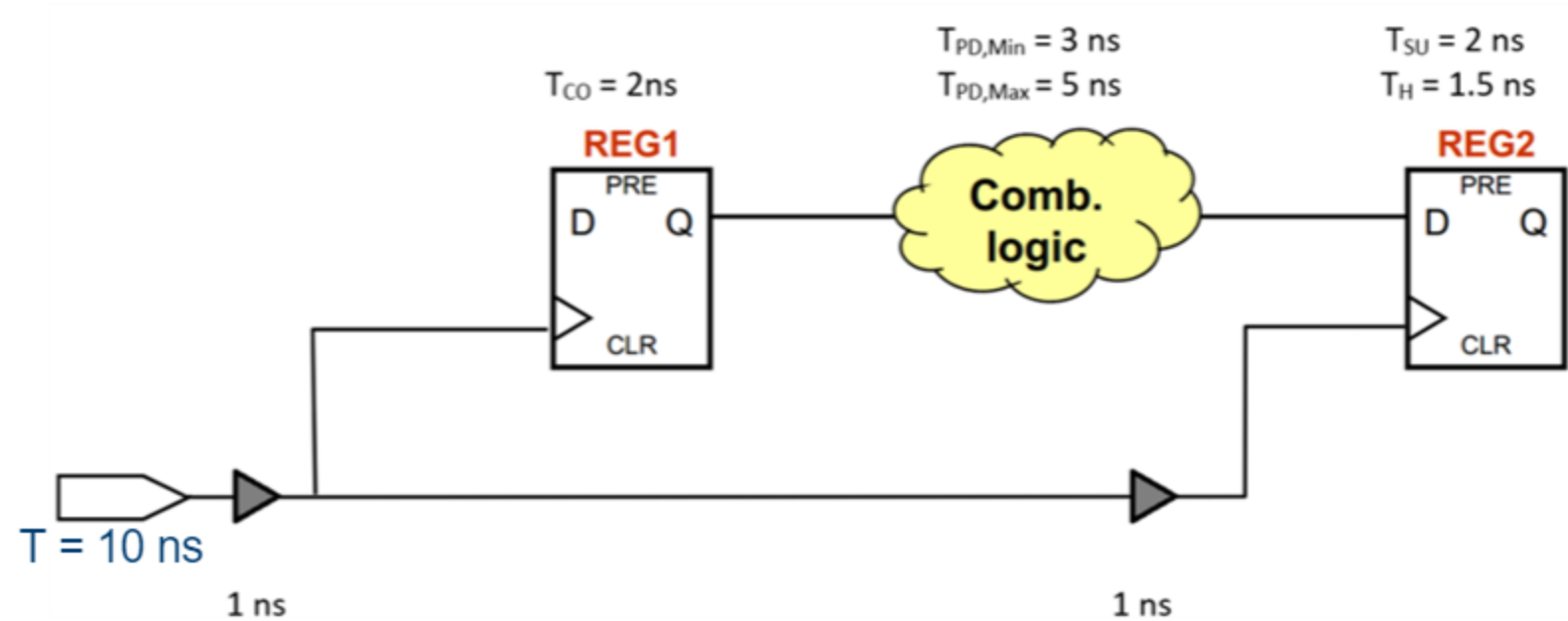

$$\text{Setup Slack} = \min \text{DRT} - \max \text{DAT} =$$

Solution


Exercise 1(a)

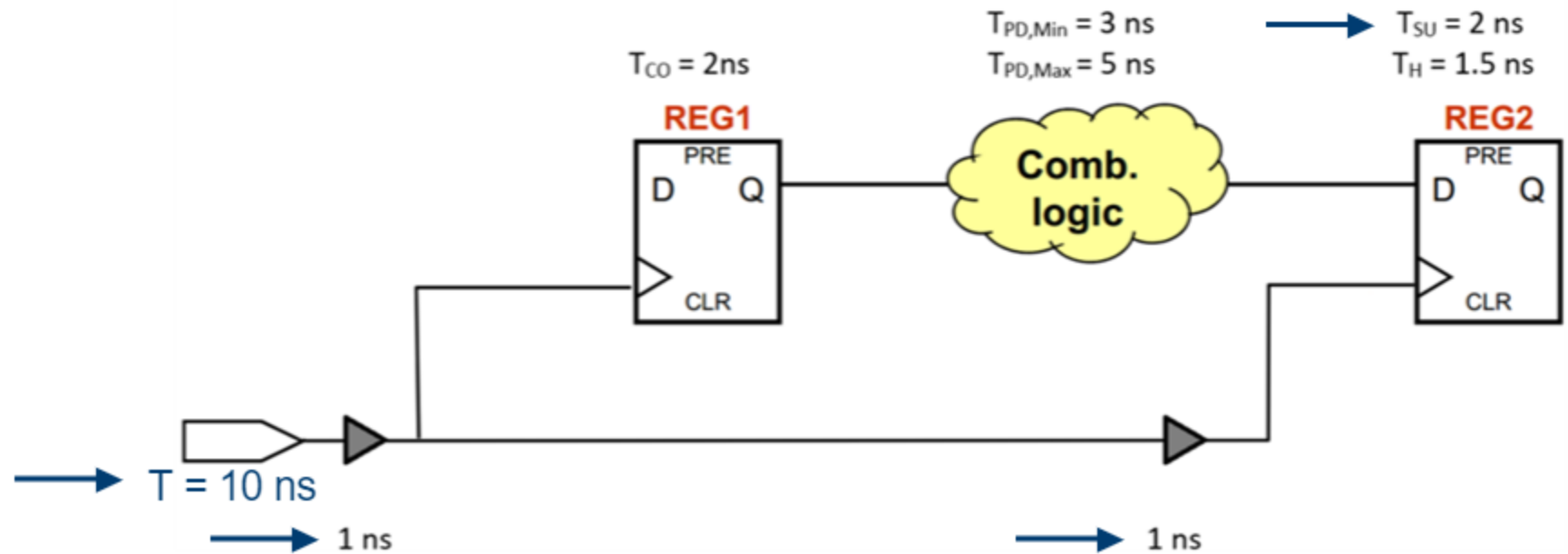

$$\text{Setup Slack} = \text{min DRT} - \text{max DAT} = (10 + 1 + 1 - 2)$$

Solution


Exercise 1(a)

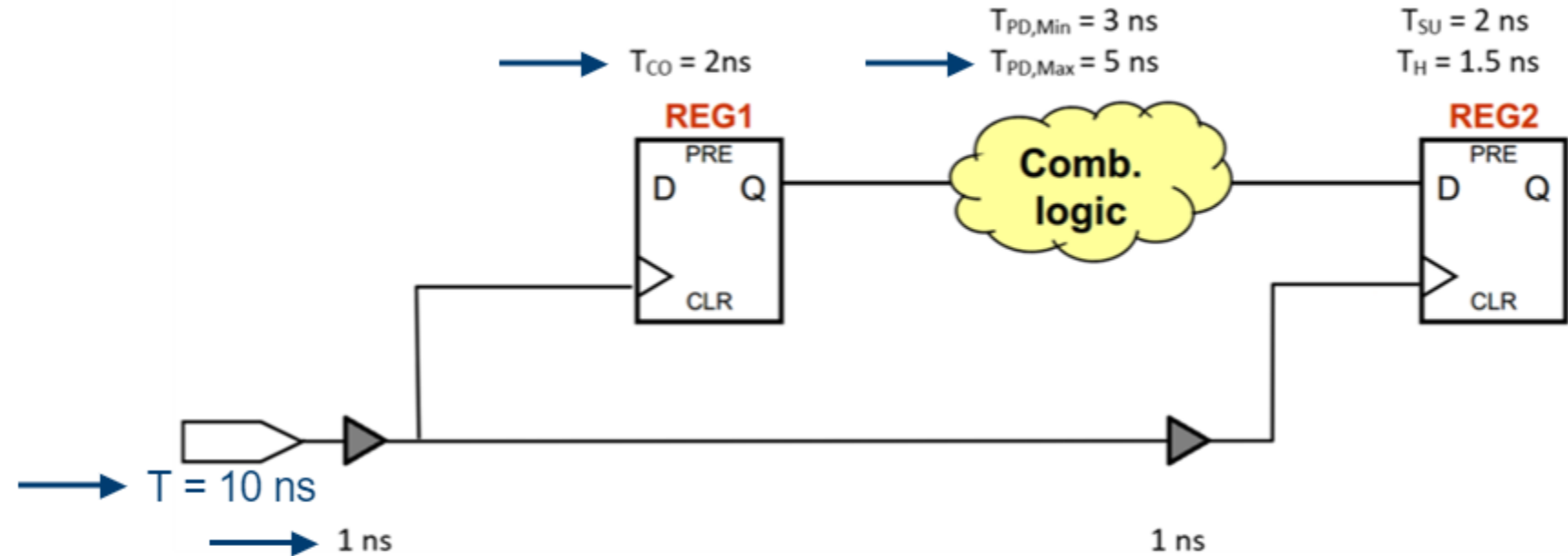

$$\text{Setup Slack} = \text{min DRT} - \text{max DAT} = (10 + 1 + 1 - 2) - (1 + 2 + 5) = 2\text{ ns}$$

Solution

Exercise 1(a)

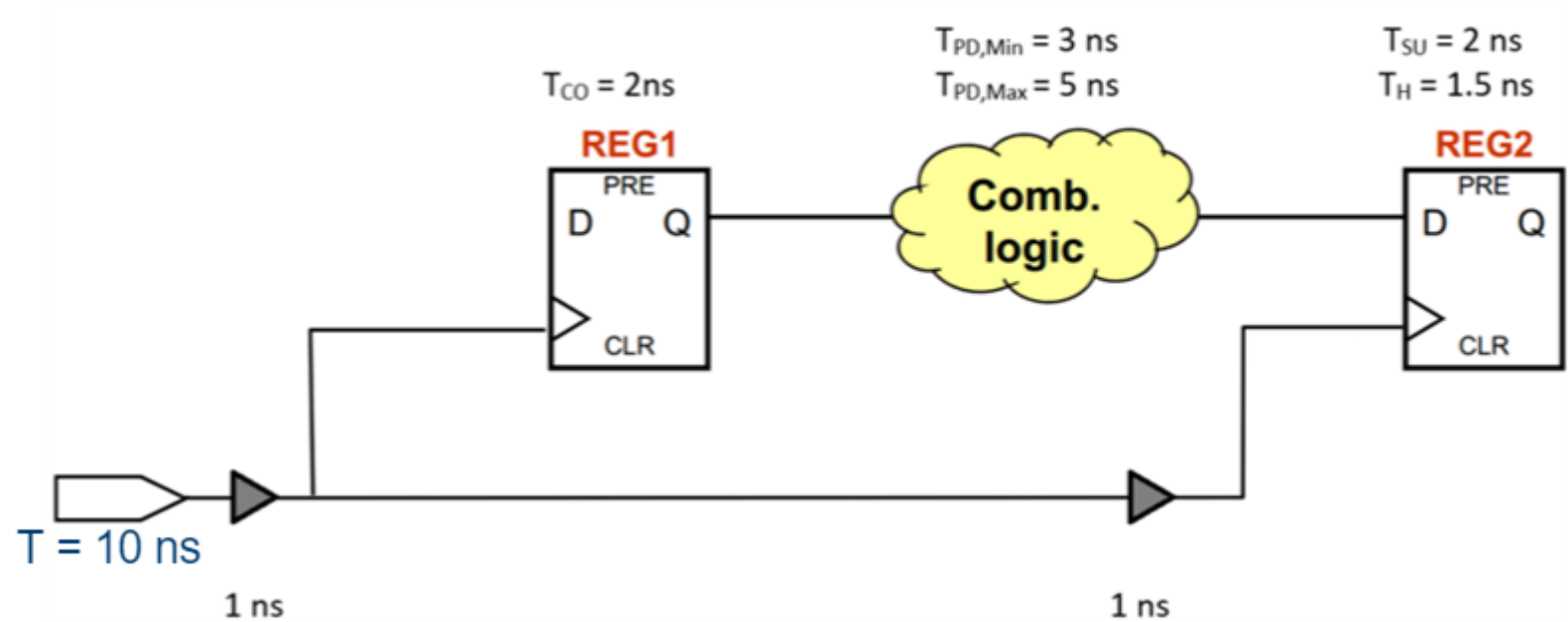


$$\text{Setup Slack} = \text{min DRT} - \text{max DAT} = (10 + 1 + 1 - 2) - (1 + 2 + 5) = 2\text{ ns}$$

$$\text{Hold Slack} = \text{min DAT} - \text{max DRT} =$$

Solution

Exercise 1(a)

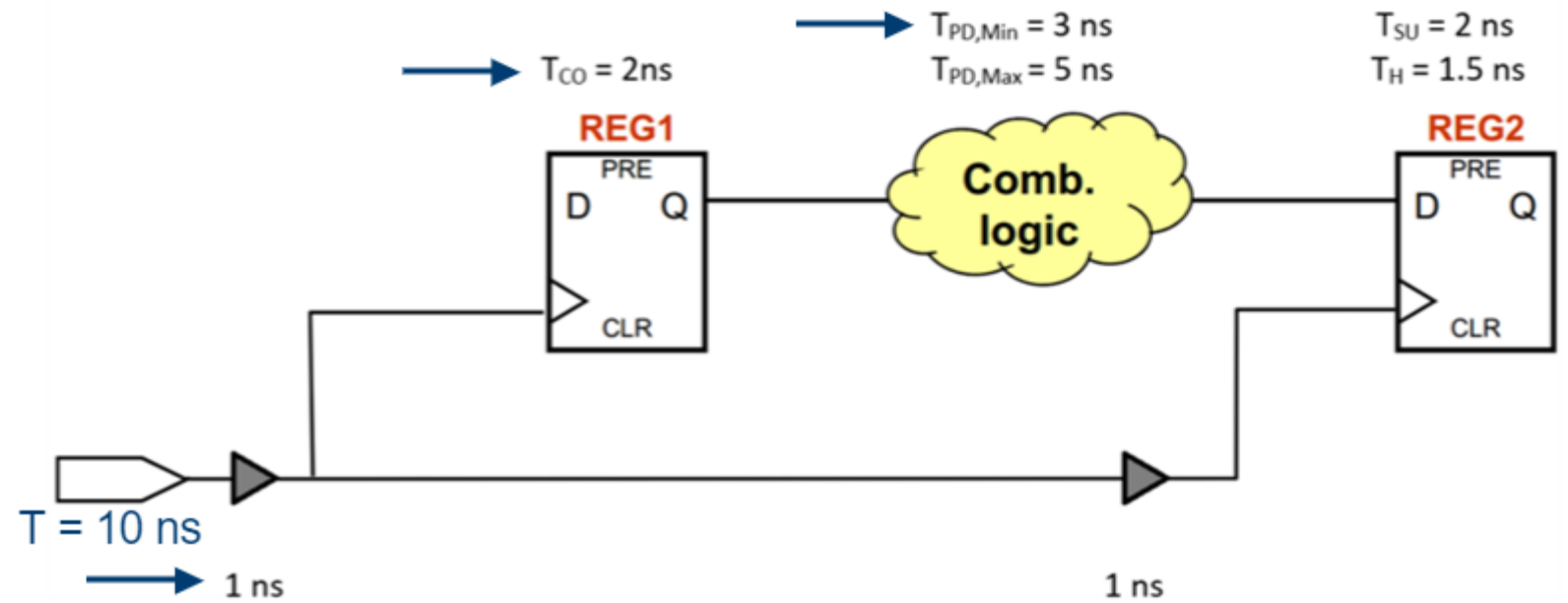


$$\text{Setup Slack} = \text{min DRT} - \text{max DAT} = (10 + 1 + 1 - 2) - (1 + 2 + 5) = 2\text{ ns}$$

$$\text{Hold Slack} = \text{min DAT} - \text{max DRT} = (1 + 2 + 3)$$

Solution

Exercise 1(a)

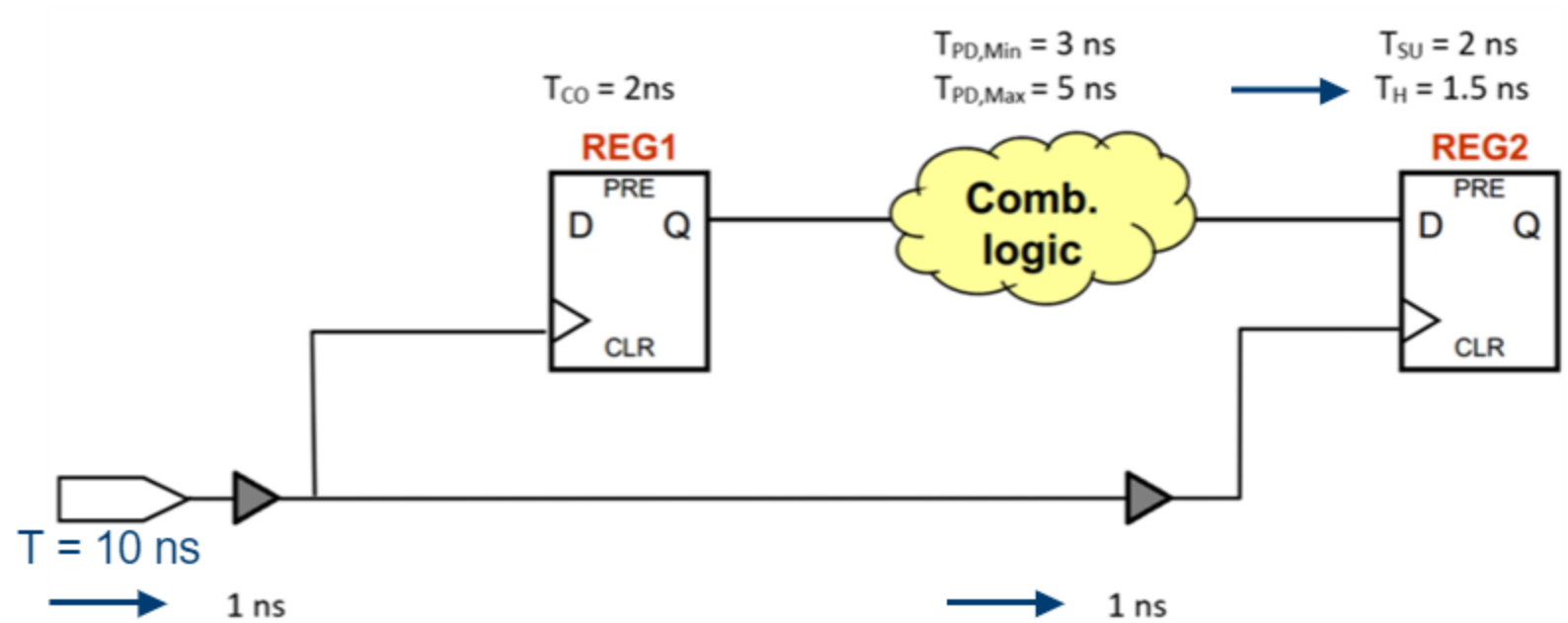


$$\text{Setup Slack} = \text{min DRT} - \text{max DAT} = (10 + 1 + 1 - 2) - (1 + 2 + 5) = 2\text{ ns}$$

$$\text{Hold Slack} = \text{min DAT} - \text{max DRT} = (1 + 2 + 3) - (1 + 1 + 1.5) = 2.5\text{ ns}$$

Solution

Exercise 1(b)

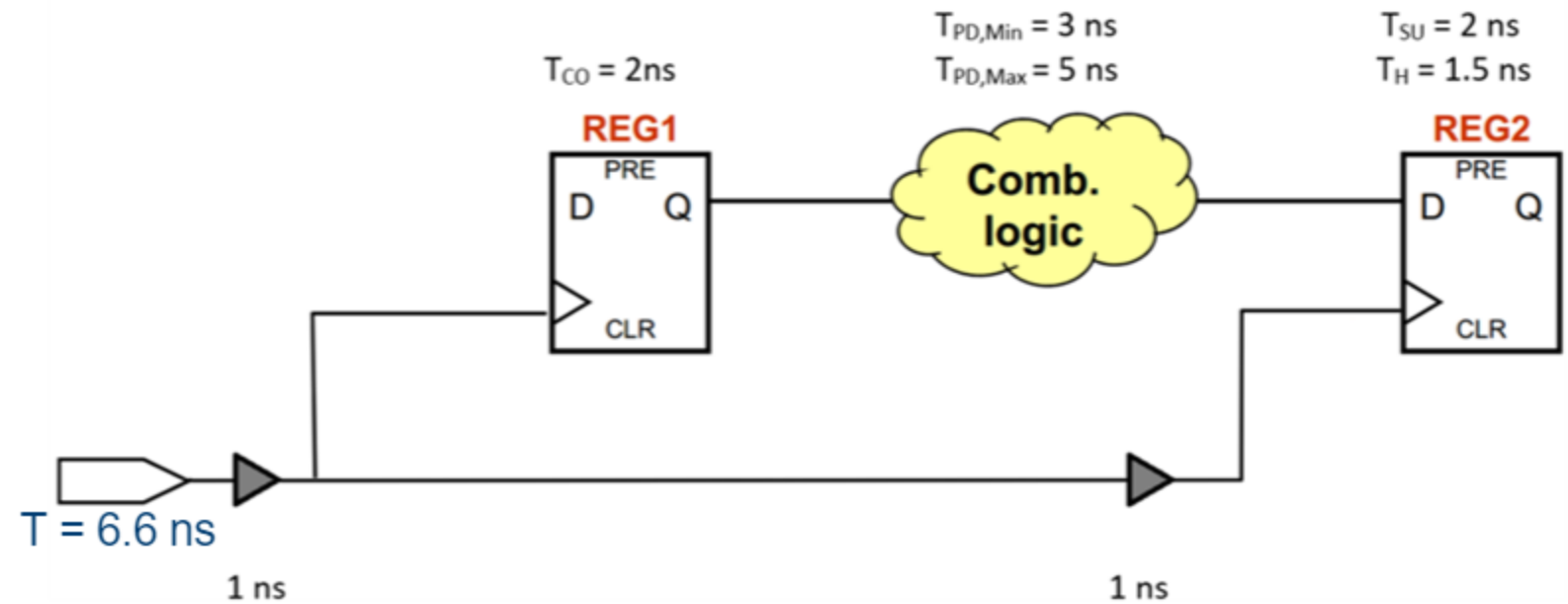


Setup Slack = min DRT – max DAT =

Hold Slack = min DAT – max DRT =

Solution

Exercise 1(b)

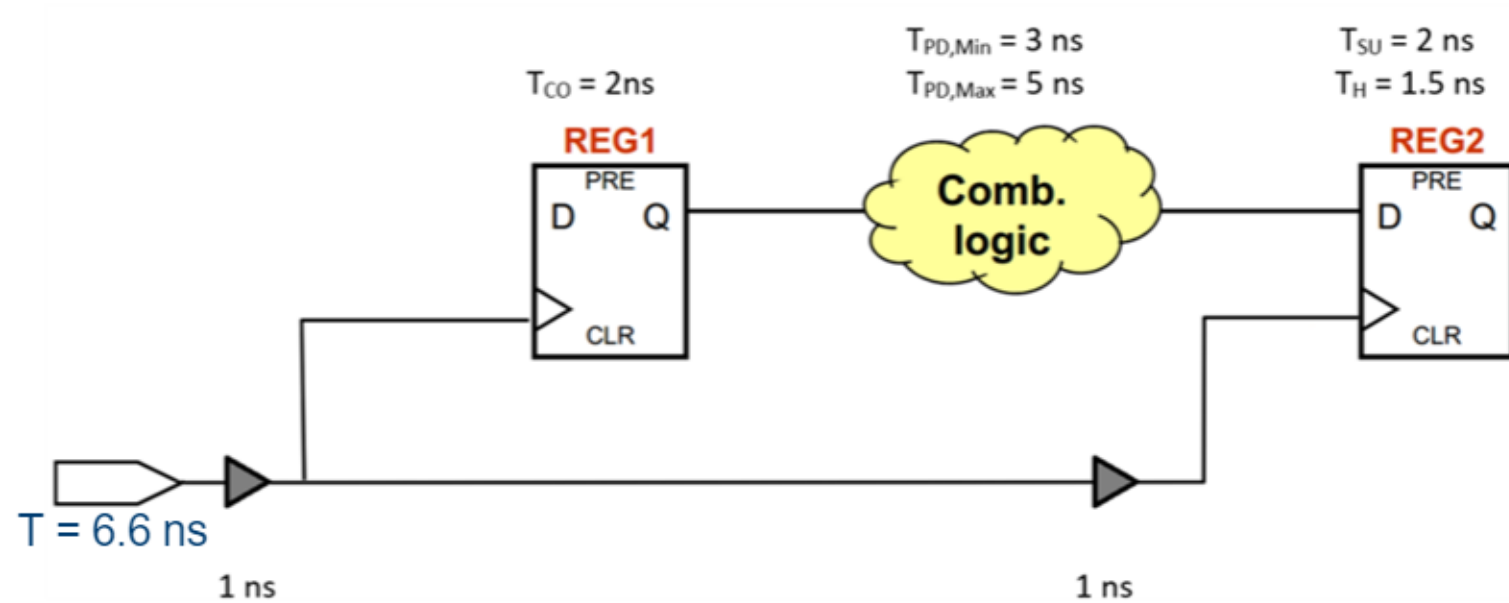

$$\text{Setup Slack} = \text{min DRT} - \text{max DAT} = (6.6 + 1 + 1 - 2) - (1 + 2 + 5) = -1.4 \text{ (Fails!)}$$


$$\text{Hold Slack} = \text{min DAT} - \text{max DRT} = (6.6 + 1 + 2 + 3) - (6.6 + 1 + 1 + 1.5) = 2.5 \text{ ns}$$

(Doesn't change!)

Maximum Clock Frequency

- The clock frequency for a synchronous sequential circuit is limited by the timing parameters of its flip-flops and gates.
- This limit is called *the maximum clock frequency* for the circuit.
- The *minimum clock period* is the reciprocal of this frequency.
- Relevant timing parameters
 - Gates:
 - Propagation delays: $\min t_{PLH}$, $\min t_{PHL}$, $\max t_{PLH}$, $\max t_{PHL}$
 - Flip-Flops:
 - Propagation delays: $\min t_{PLH}$, $\min t_{PHL}$, $\max t_{PLH}$, $\max t_{PHL}$
 - Setup time: t_{su}
 - Hold time: t_h

- Example

 


$$T_W \geq \max t_{PFF} + t_{su}$$

□ Assume, $\max t_{PLH} = 25\text{ns}$, $\max t_{PHL} = 40\text{ns}$, $t_{su} = 20\text{ns}$

$$T_W \geq \max (\max t_{PLH} + t_{su}, \max t_{PHL} + t_{su})$$



$$T_W \geq \max (25+20, 40+20) = 60$$

- Example

 


$$T_W \geq \max t_{PFF} + \max t_{PINV} + t_{su}$$

- Example

 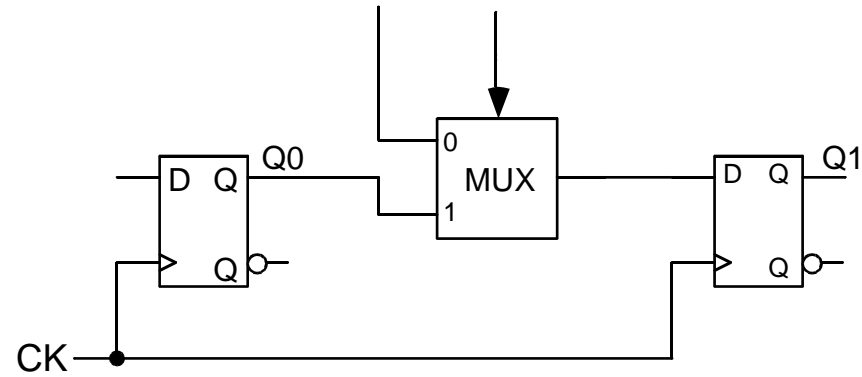

$$T_W \geq \max t_{PFF} + \max t_{PMUX} + t_{su}$$

- Example

 

	t_p	t_{su}
D Flip-Flop:	20 ns	5 ns
JK Flip-Flop:	25 ns	10 ns
AND Gate:	12 ns	
OR Gate:	10 ns	

Paths from Q1 to Q1: None

Paths from Q1 to Q2: $T_W \geq \max t_{PDFF} + t_{JKsu} = 20 + 10 = 30 \text{ ns}$

$T_W \geq \max t_{PDFF} + \max t_{AND} + t_{JKsu} = 20 + 12 + 10 = 42 \text{ ns}$

Paths from Q2 to Q1: $T_W \geq \max t_{PJKFF} + t_{OR} + T_{Dsu} = 25 + 10 + 5 = 40 \text{ ns}$

Paths from Q2 to Q2: $T_W \geq \max t_{PJKFF} + \max t_{AND} + t_{JKsu} = 25 + 12 + 10 = 47 \text{ ns}$

$T_W \geq 47 \text{ ns}$